


4 BIT ADDER/SUBTRACTOR

INPUT NUMBER SYSTEM: BASE 4

OUTPUT NUMBER SYSTEM: BASE 4

Checklist:

- Both input and output will be display on 7 Segment display devices with respect to their base system
- Design would have a switch to enter into a signed or unsigned system.
 - Signed system: A system which includes both (+) and (-) numbers, thus, in a 4 bits system, the number would be from -8..7.
 - Unsigned System: A system which includes only (+), thus, in a 4 bits system, the number would be from 0..15.

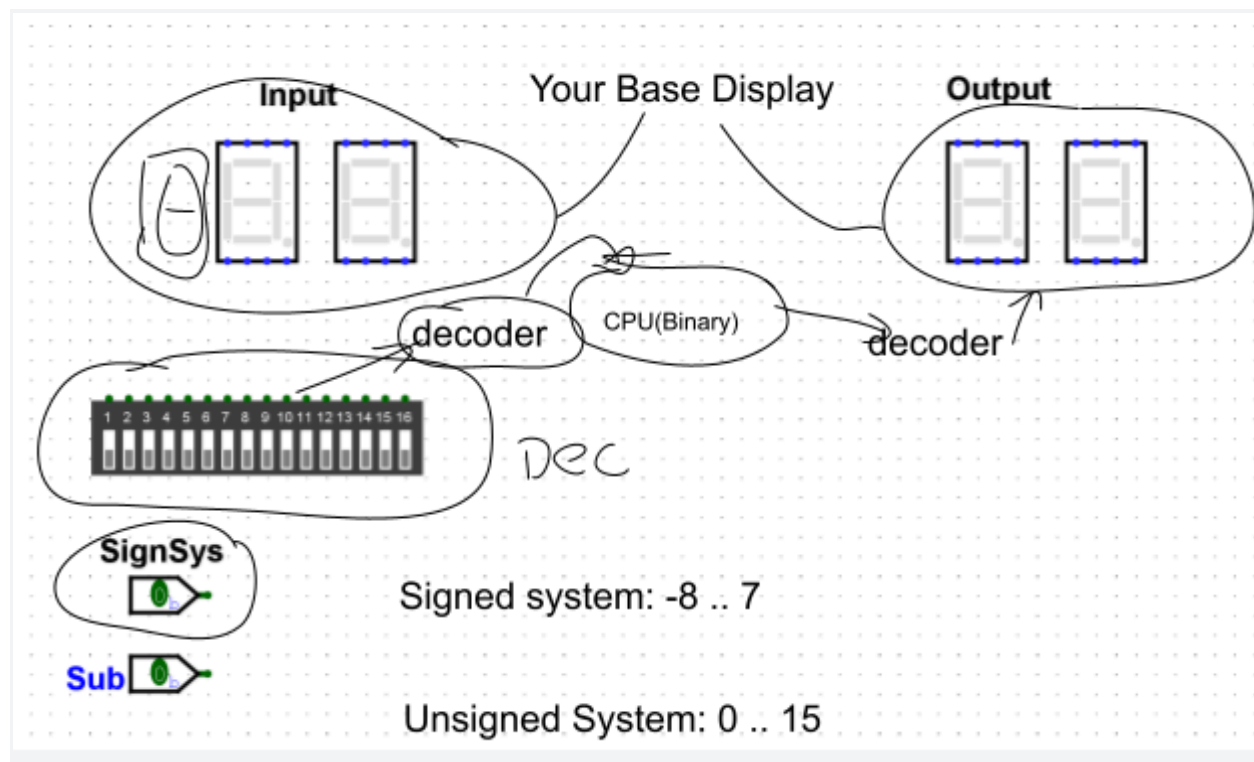


MUX Design

1. Adder and Subtractor MUX (insert its working log here(truthtable, kmap and etc) and logisim design)


Truth Table:

A	not A	Cin (0 = add, 1 = sub)	MUX Output
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0

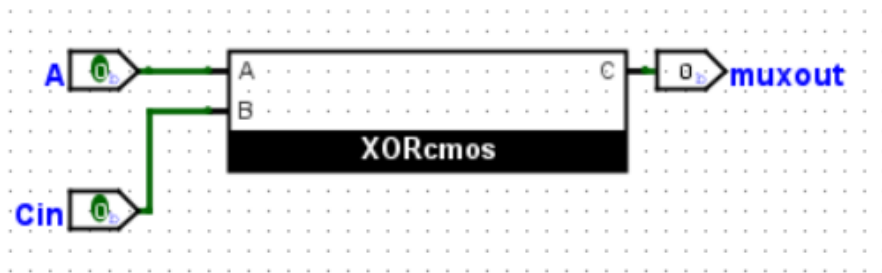Reduce 3 inputs into 2 input; MUX Output = A XOR Cin



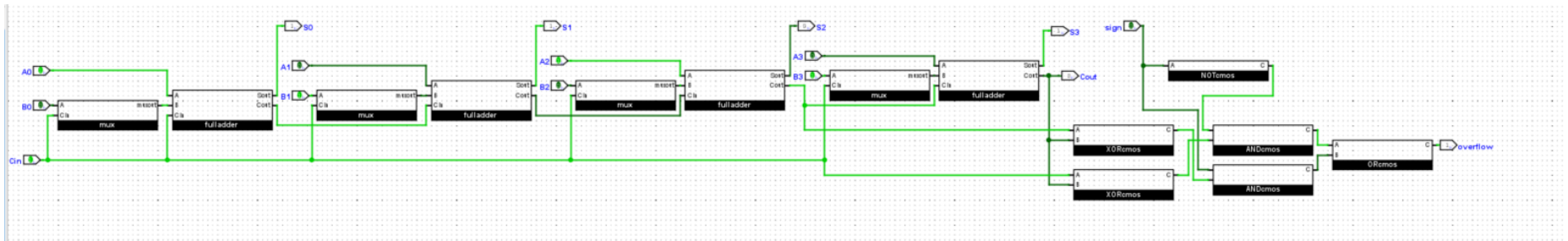Four bit adder/subtractor with signed/unsigned system and overflow:



Decoder Design

1. Input Decoder

SIGNED:

Convert decimal to binary (mapping): 16 inputs (-8 to 7) map to 4 outputs (4 bits of binary number)

Decimal	-8	-7	-6	-5	-4	-3	-2	-1	0	1	2	3	4	5	6	7
Input Letter	A	B	C	D	E	F	G	H	I	J	K	L	M	N	O	P
Binary (4 bit 2's comp)	1000	1001	1010	1011	1100	1101	1110	1111	0000	0001	0010	0011	0100	0101	0110	0111

Boolean equations for each bit of binary number:


$B_3 = \text{MSB}, B_0 = \text{LSB}$

$B_3 = A + B + C + D + E + F + G + H$

$B_2 = E + F + G + H + M + N + O + P$

$$B_1 = C + D + G + H + K + L + O + P$$

$$B_0 = B + D + F + H + J + L + N + P$$

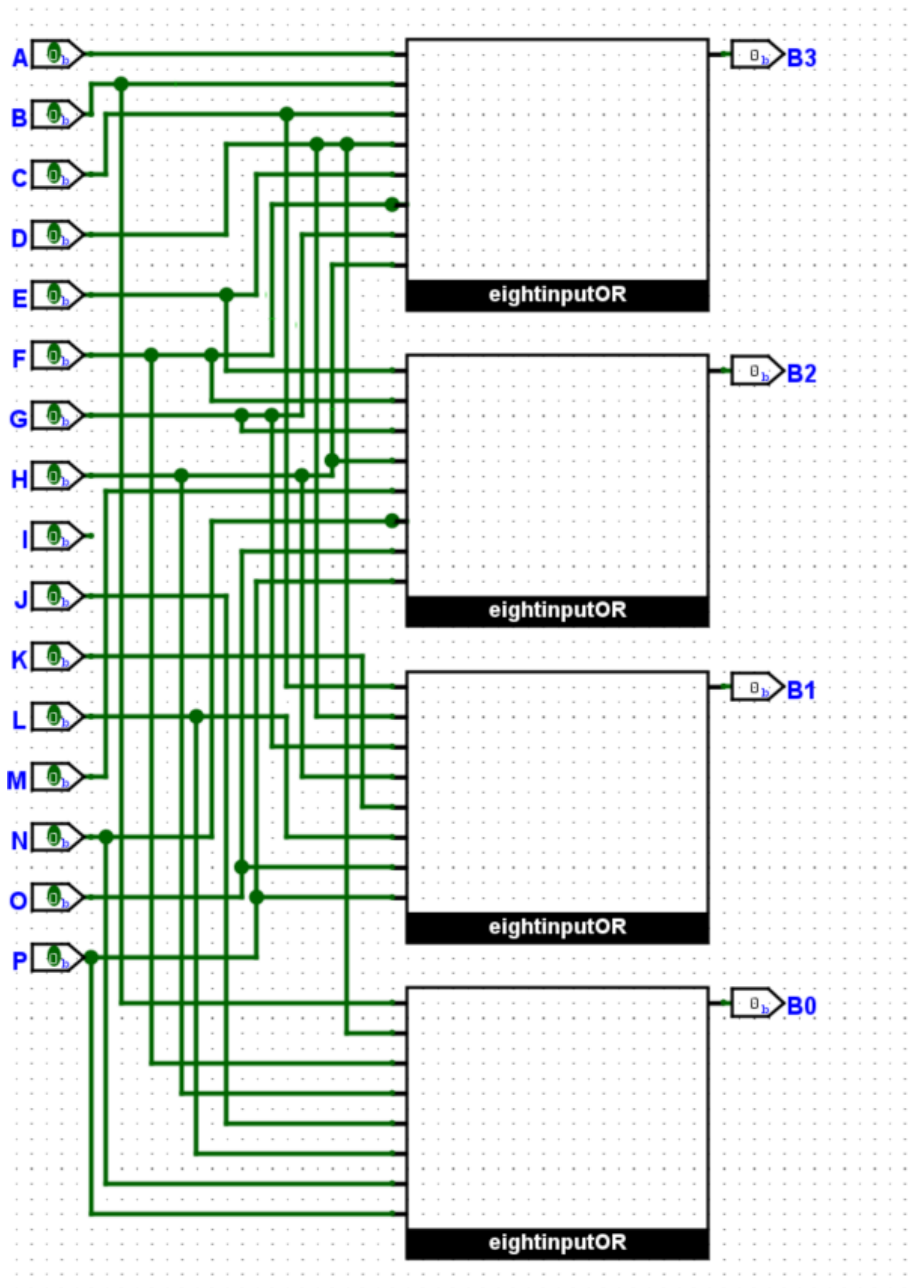

UNSIGNED:

Decimal	0	1	2	3	4	5	6	7	8	9	10	11	12	13	14	15
Input Letter	A	B	C	D	E	F	G	H	I	J	K	L	M	N	O	P
Binary (4 bit 2's comp)	0000	0001	0010	0011	0100	0101	0110	0111	1000	1001	1010	1011	1100	1101	1110	1111

Boolean equations for each bit of binary number:


$B_3 = \text{MSB}, B_0 = \text{LSB}$

$$B_3 = I + J + K + L + M + N + O + P$$


$$B_2 = E + F + G + H + M + N + O + P$$

$$B_1 = C + D + G + H + K + L + O + P$$

$$B_0 = B + D + F + H + J + L + N + P$$

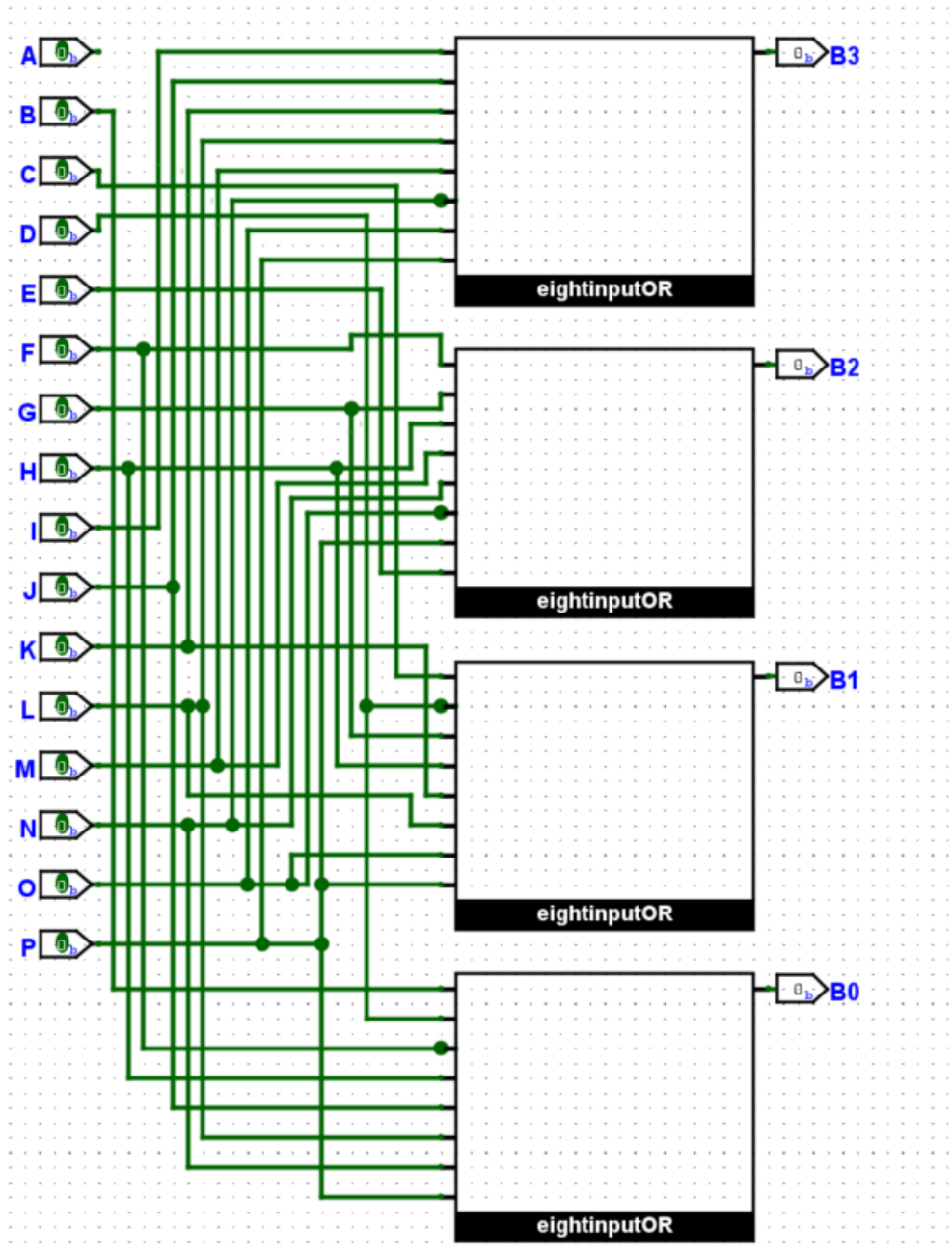

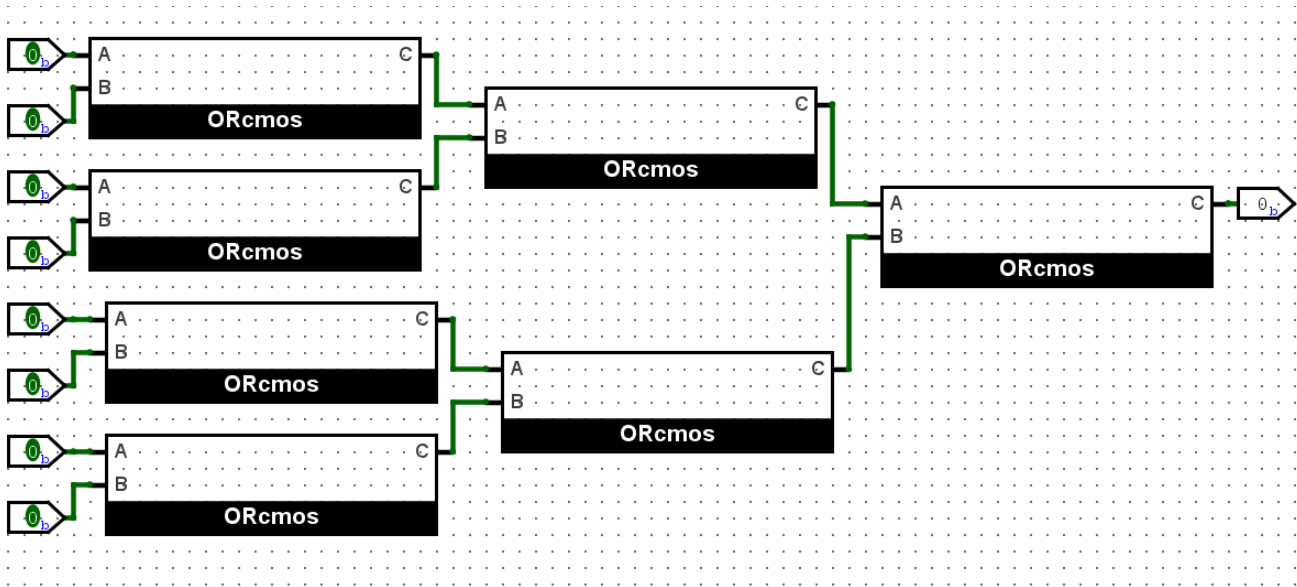Custom 8-input OR Gate (because every boolean equation is 8 ORs):



4-bit MUX

Toggle between the signed vs unsigned value based on the sign value

Inputs: A3, A2, A1, A0 (unsigned values), B3, B2, B1, B0 (signed values), sign=0 for unsigned, sign=1 for signed

Output: C3, C2, C1, C0 → correct value


Boolean equations:

$$C3 = (A3 * \overline{sign}) + (B3 * sign)$$

$$C2 = (A2 * \overline{sign}) + (B2 * sign)$$

$$C1 = (A1 * \overline{sign}) + (B1 * sign)$$
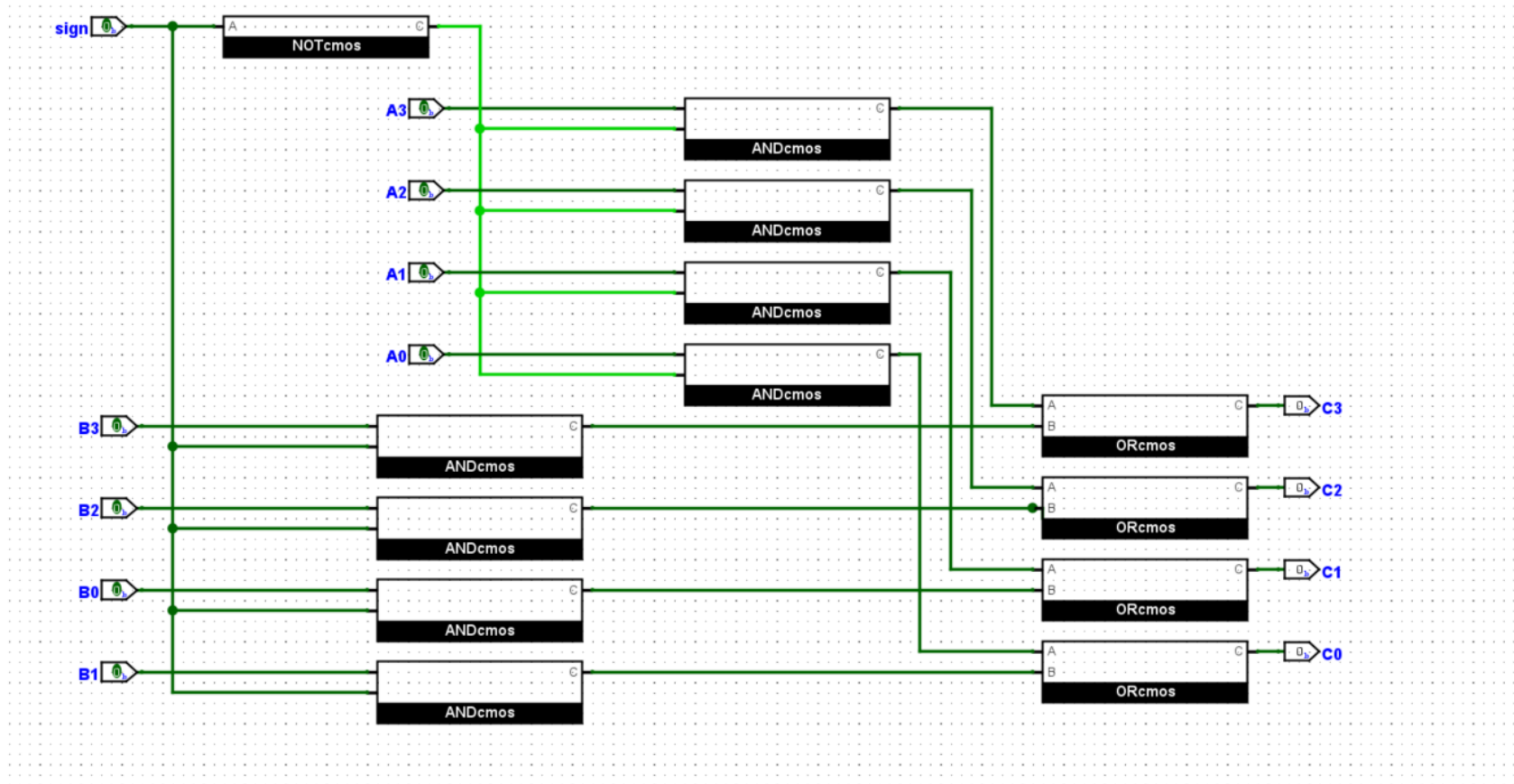
$$C0 = (A0 * \overline{sign}) + (B0 * sign)$$




2. Output Decoder

4 inputs: 4 bits of binary number B0, B1, B2, B3, B3 MSB, B0 LSB

SIGNED:

Truth Table:

B3	B2	B1	B0	Decimal	Output Letter	Boolean Equation
1	0	0	0	-8	A	$\overline{B0} * \overline{B1} * \overline{B2} * B3$
1	0	0	1	-7	B	$B0 * \overline{B1} * \overline{B2} * B3$
1	0	1	0	-6	C	$\overline{B0} * B1 * \overline{B2} * B3$
1	0	1	1	-5	D	$B0 * B1 * \overline{B2} * B3$
1	1	0	0	-4	E	$\overline{B0} * \overline{B1} * B2 * B3$
1	1	0	1	-3	F	$B0 * \overline{B1} * B2 * B3$
1	1	1	0	-2	G	$\overline{B0} * B1 * B2 * B3$
1	1	1	1	-1	H	$B0 * B1 * B2 * B3$
0	0	0	0	0	I	$\overline{B0} * \overline{B1} * \overline{B2} * \overline{B3}$
0	0	0	1	1	J	$B0 * \overline{B1} * \overline{B2} * \overline{B3}$
0	0	1	0	2	K	$\overline{B0} * B1 * \overline{B2} * \overline{B3}$
0	0	1	1	3	L	$B0 * B1 * \overline{B2} * \overline{B3}$
0	1	0	0	4	M	$\overline{B0} * \overline{B1} * B2 * \overline{B3}$
0	1	0	1	5	N	$B0 * \overline{B1} * B2 * \overline{B3}$
0	1	1	0	6	O	$\overline{B0} * B1 * B2 * \overline{B3}$
0	1	1	1	7	P	$B0 * B1 * B2 * \overline{B3}$

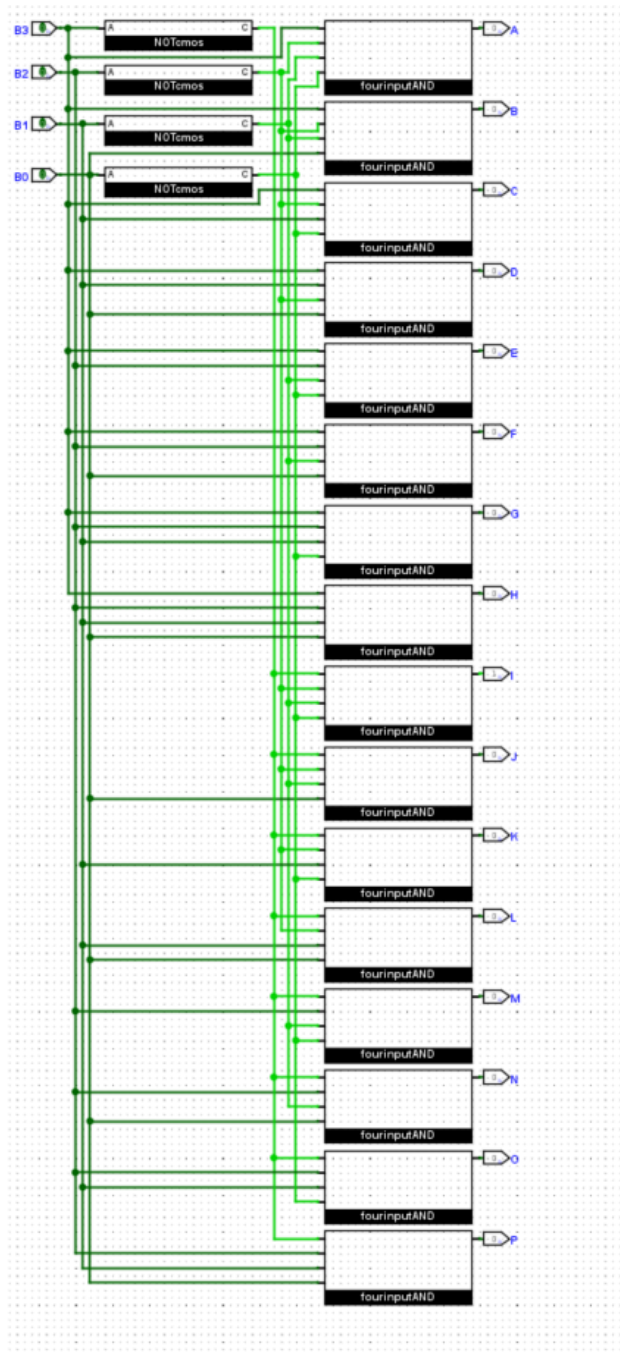


UNSIGNED:

Truth Table:


B3	B2	B1	B0	Decimal	Output Letter	Boolean Equation
0	0	0	0	0	A	$\overline{B0} * \overline{B1} * \overline{B2} * \overline{B3}$
0	0	0	1	1	B	$B0 * \overline{B1} * \overline{B2} * \overline{B3}$
0	0	1	0	2	C	$\overline{B0} * B1 * \overline{B2} * \overline{B3}$
0	0	1	1	3	D	$B0 * B1 * \overline{B2} * \overline{B3}$
0	1	0	0	4	E	$\overline{B0} * \overline{B1} * B2 * \overline{B3}$
0	1	0	1	5	F	$B0 * \overline{B1} * B2 * \overline{B3}$
0	1	1	0	6	G	$\overline{B0} * B1 * B2 * \overline{B3}$
0	1	1	1	7	H	$B0 * B1 * B2 * \overline{B3}$
1	0	0	0	8	I	$\overline{B0} * \overline{B1} * \overline{B2} * B3$
1	0	0	1	9	J	$B0 * \overline{B1} * \overline{B2} * B3$
1	0	1	0	10	K	$\overline{B0} * B1 * \overline{B2} * B3$
1	0	1	1	11	L	$B0 * B1 * \overline{B2} * B3$
1	1	0	0	12	M	$\overline{B0} * \overline{B1} * B2 * B3$
1	1	0	1	13	N	$B0 * \overline{B1} * B2 * B3$



1	1	1	0	14	O	$\overline{B0} * B1 * B2 * B3$
1	1	1	1	15	P	$B0 * B1 * B2 * B3$

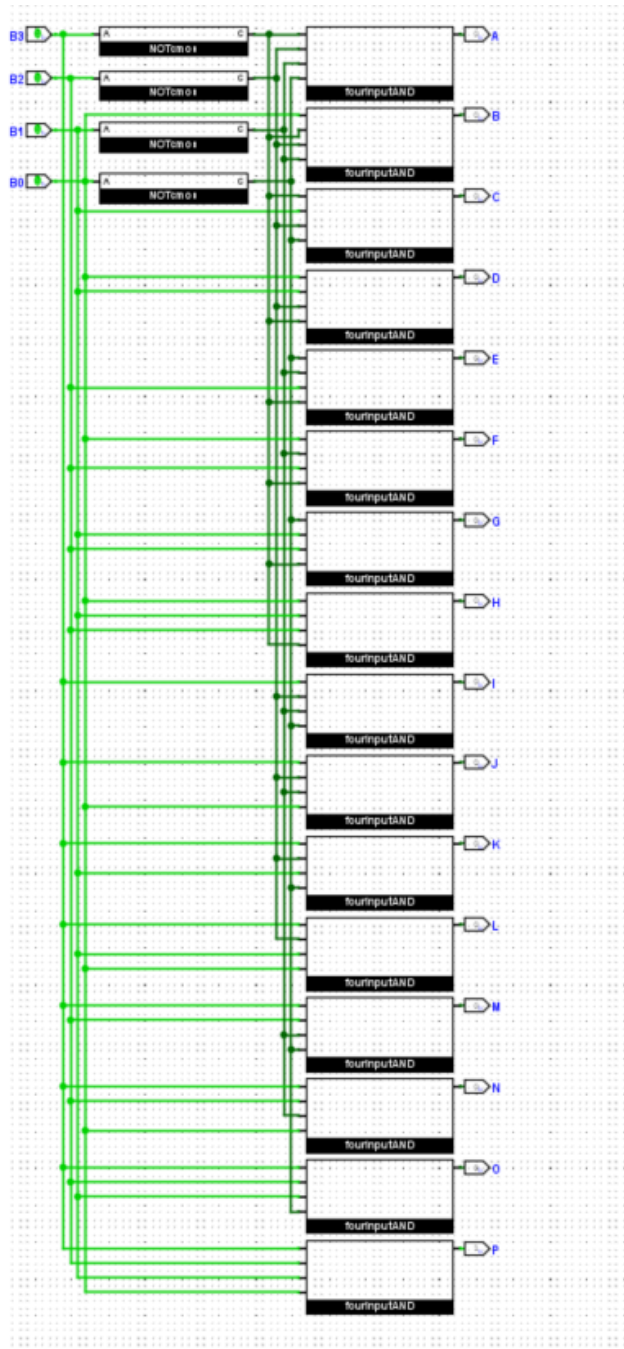

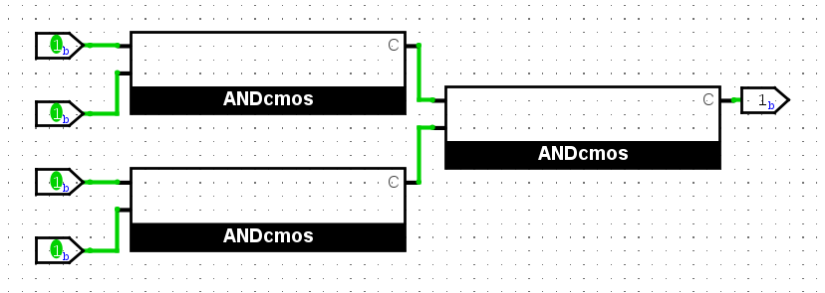Custom 4-input AND gate (every boolean equation is 4 ANDs):



16-bit MUX

Toggle between the signed vs unsigned value based on the sign value

Inputs: A0, B0, C0, D0, E0, F0, ... P0 (unsigned values), A1, B1, C1, D1, E1, F1, ... P1 (signed values), sign=0 for unsigned, sign=1 for signed

Output: A, B, C, D, E, ... P → correct value

Boolean equations:

$$A = (A0 * \overline{sign}) + (A1 * sign)$$



$$B = (B0 * \overline{sign}) + (B1 * sign)$$

$$B = (B0 * \overline{sign}) + (B1 * sign)$$

...

$$P = (P0 * \overline{sign}) + (P1 * sign)$$

7 Segment

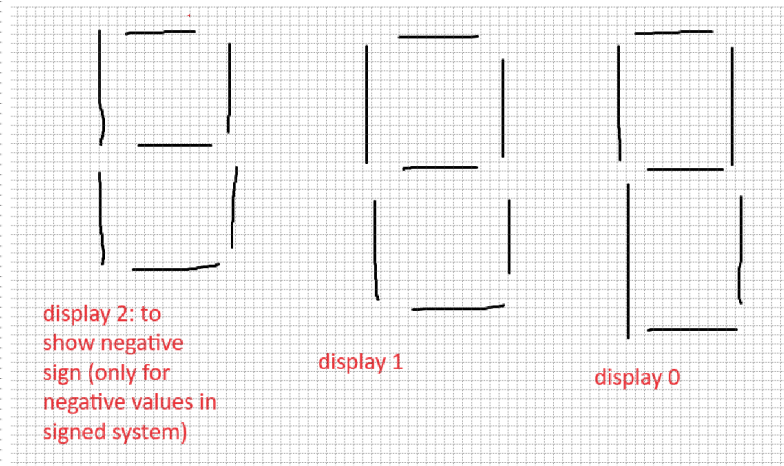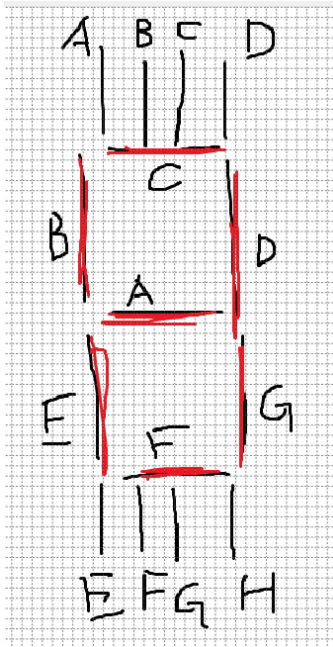

Input (map decimal to base 4)

Digit	A	B	C	D	E	F	G
0	0	1	1	1	1	1	1
1	0	0	0	1	0	0	1
2	1	0	1	1	1	1	0
3	1	0	1	1	0	1	1

SIGNED:

	Base 10	Base 4		Display 1							Display 0						
			A2	A1	B1	C1	D1	E1	F1	G1	A0	B0	C0	D0	E0	F0	G0
A	-8	-20	1	1	0	1	1	1	1	0	0	1	1	1	1	1	1
B	-7	-13	1	0	0	0	1	0	0	1	1	0	1	1	0	1	1
C	-6	-12	1	0	0	0	1	0	0	1	1	0	1	1	1	1	0
D	-5	-11	1	0	0	0	1	0	0	1	0	0	0	1	0	0	1
E	-4	-10	1	0	0	0	1	0	0	1	0	1	1	1	1	1	1
F	-3	-03	1	0	1	1	1	1	1	1	1	0	1	1	0	1	1
G	-2	-02	1	0	1	1	1	1	1	1	1	0	1	1	1	1	0
H	-1	-01	1	0	1	1	1	1	1	1	0	0	0	1	0	0	1
I	0	00	0	0	1	1	1	1	1	1	0	1	1	1	1	1	1
J	1	01	0	0	1	1	1	1	1	1	0	0	0	1	0	0	1
K	2	02	0	0	1	1	1	1	1	1	1	0	1	1	1	1	0
L	3	03	0	0	1	1	1	1	1	1	1	0	1	1	0	1	1
M	4	10	0	0	0	0	1	0	0	1	0	1	1	1	1	1	1
N	5	11	0	0	0	0	1	0	0	1	0	0	0	1	0	0	1
O	6	12	0	0	0	0	1	0	0	1	1	0	1	1	1	1	0

P	7	13	0	0	0	0	1	0	0	1	1	0	1	1	0	1	1
---	---	----	---	---	---	---	---	---	---	---	---	---	---	---	---	---	---

UNSIGNED:


Input	Base 10	Base 4		Display 1							Display 0						
			A2	A1	B1	C1	D1	E1	F1	G1	A0	B0	C0	D0	E0	F0	G0
A	0	00	0	0	1	1	1	1	1	1	0	1	1	1	1	1	1
B	1	01	0	0	1	1	1	1	1	1	0	0	0	1	0	0	1
C	2	02	0	0	1	1	1	1	1	1	1	0	1	1	1	1	0
D	3	03	0	0	1	1	1	1	1	1	1	0	1	1	0	1	1
E	4	10	0	0	0	0	1	0	0	1	0	1	1	1	1	1	1
F	5	11	0	0	0	0	1	0	0	1	0	0	0	1	0	0	1
G	6	12	0	0	0	0	1	0	0	1	1	0	1	1	1	1	0
H	7	13	0	0	0	0	1	0	0	1	1	0	1	1	0	1	1
I	8	20	0	1	0	1	1	1	1	0	0	1	1	1	1	1	1
J	9	21	0	1	0	1	1	1	1	0	0	0	0	1	0	0	1
K	10	22	0	1	0	1	1	1	1	0	1	0	1	1	1	1	0
L	11	23	0	1	0	1	1	1	1	0	1	0	1	1	0	1	1
M	12	30	0	1	0	1	1	0	1	1	0	1	1	1	1	1	1
N	13	31	0	1	0	1	1	0	1	1	0	0	0	1	0	0	1

O	14	32	0	1	0	1	1	0	1	1	1	0	1	1	1	1	0
P	15	33	0	1	0	1	1	0	1	1	1	0	1	1	0	1	1

Using truth table, map using boolean equation by OR the letter inputs that turn each segment on

MUX: $\text{segOn} = (\text{signedMap}() * \text{sign}) + (\text{unsignedMap}() * (\text{not sign}))$

Full circuit (signed + unsigned + MUX):

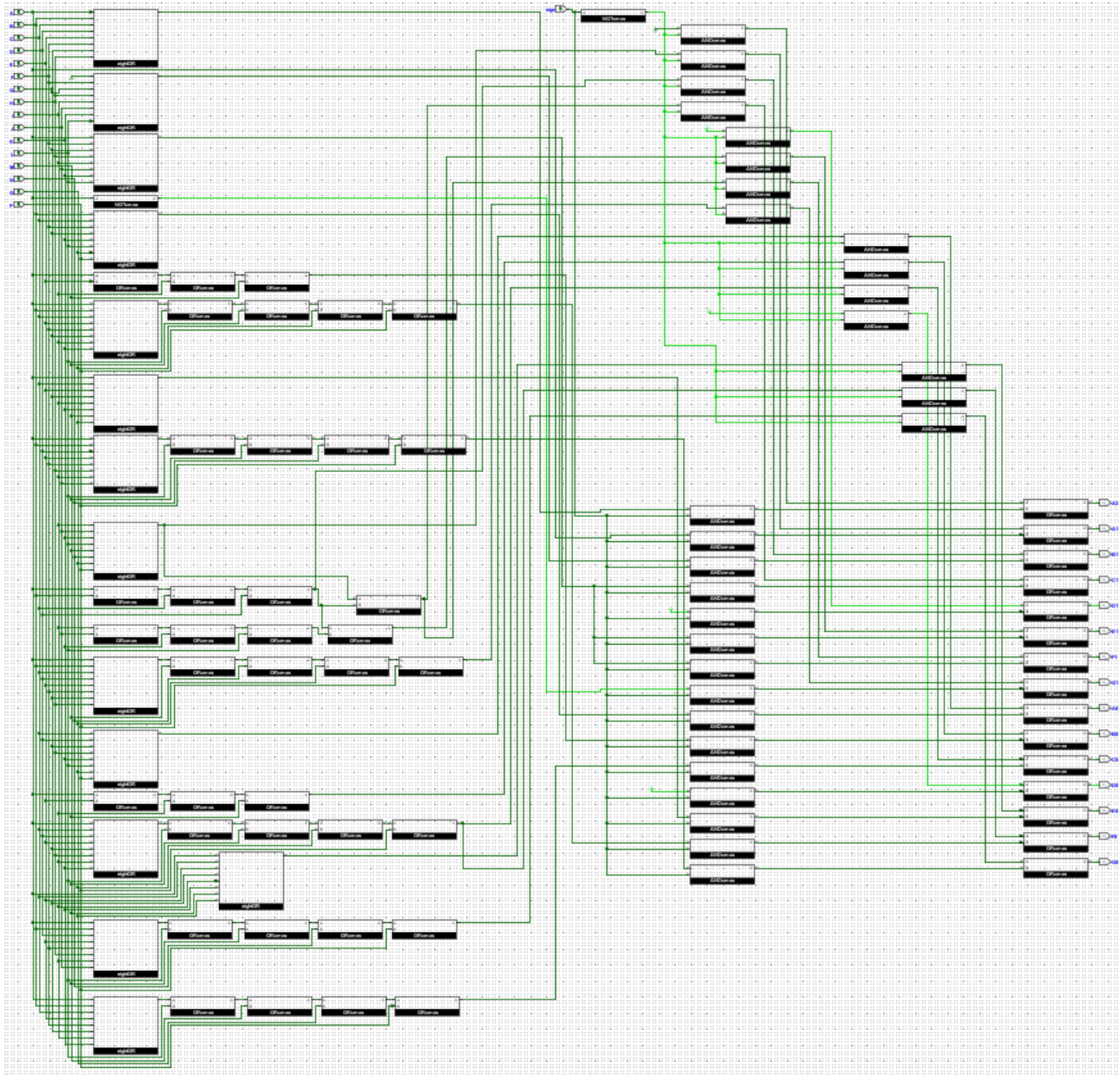


Output (map decimal to base 3)

Digit	A	B	C	D	E	F	G
0	0	1	1	1	1	1	1
1	0	0	0	1	0	0	1
2	1	0	1	1	1	1	0

SIGNED:

Input	Base 10	Base 3	Display 2			Display 1							Display 0						
			A2	D2	G2	A1	B1	C1	D1	E1	F1	G1	A0	B0	C0	D0	E0	F0	G0
A	-8	-22	1			1	0	1	1	1	1	0	1	0	1	1	1	1	0
B	-7	-21	1			1	0	1	1	1	1	0	0	0	0	1	0	0	1
C	-6	-20	1			1	0	1	1	1	1	0	0	1	1	1	1	1	1
D	-5	-12	1			0	0	0	1	0	0	1	1	0	1	1	1	1	0
E	-4	-11	1			0	0	0	1	0	0	1	0	0	0	1	0	0	1
F	-3	-10	1			0	0	0	1	0	0	1	0	1	1	1	1	1	1
G	-2	-02	1			0	1	1	1	1	1	1	1	0	1	1	1	1	0
H	-1	-01	1			0	1	1	1	1	1	1	0	0	0	1	0	0	1
I	0	00				0	1	1	1	1	1	1	0	1	1	1	1	1	1


J	1	01				0	1	1	1	1	1	1	0	0	0	1	0	0	1
K	2	02				0	1	1	1	1	1	1	1	0	1	1	1	1	0
L	3	10				0	0	0	1	0	0	1	0	1	1	1	1	1	1
M	4	11				0	0	0	1	0	0	1	0	0	0	1	0	0	1
N	5	12				0	0	0	1	0	0	1	1	0	1	1	1	1	0
O	6	20				1	0	1	1	1	1	0	0	1	1	1	1	1	1
P	7	21				1	0	1	1	1	1	0	0	0	0	1	0	0	1

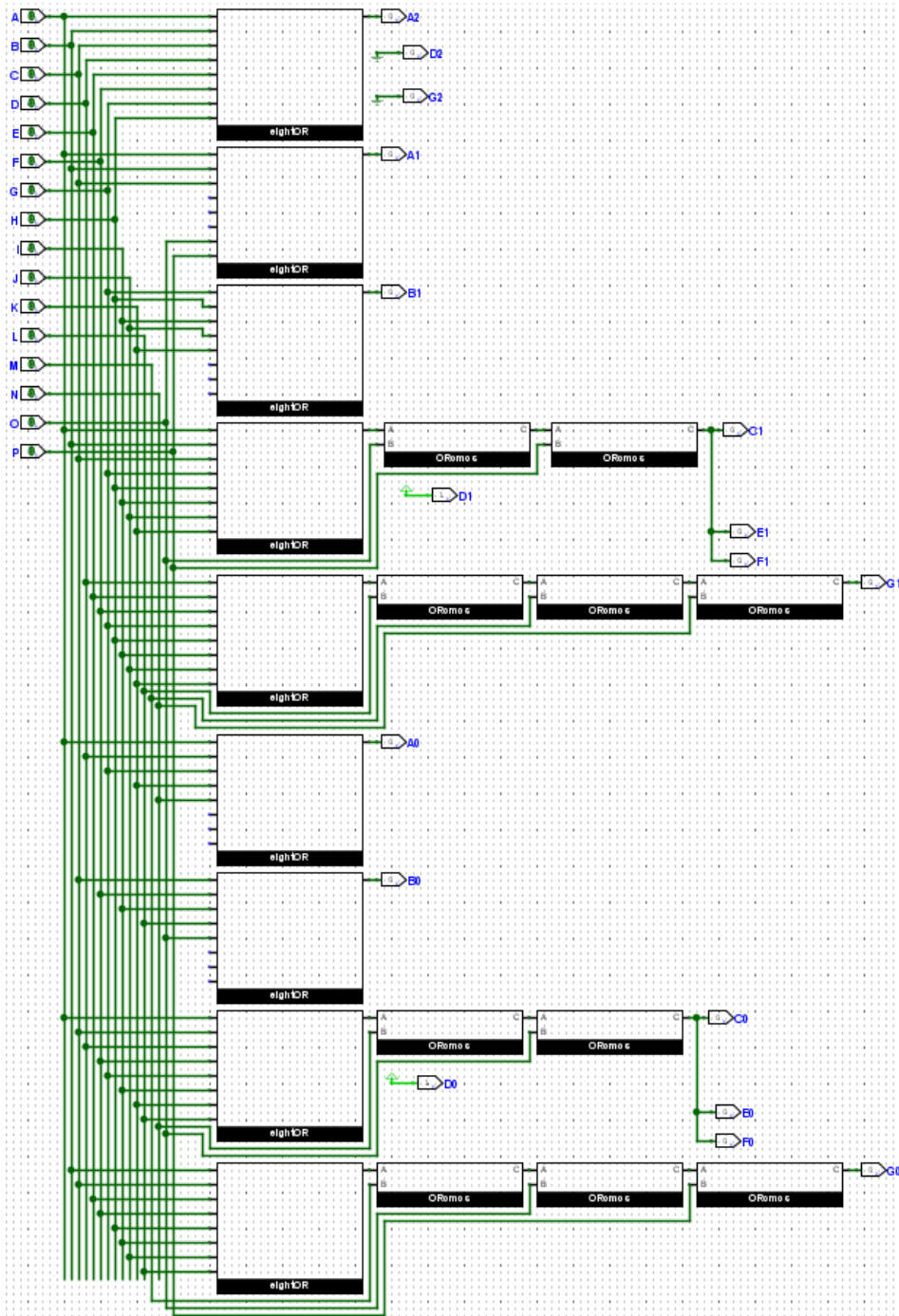

UNSIGNED:


Input	Base 10	Base 3	Display 2			Display 1							Display 0						
			A2	D2	G2	A1	B1	C1	D1	E1	F1	G1	A0	B0	C0	D0	E0	F0	G0
A	0	00				0	1	1	1	1	1	1	0	1	1	1	1	1	1
B	1	01				0	1	1	1	1	1	1	0	0	0	1	0	0	1
C	2	02				0	1	1	1	1	1	1	1	0	1	1	1	1	0
D	3	10				0	0	0	1	0	0	1	0	1	1	1	1	1	1
E	4	11				0	0	0	1	0	0	1	0	0	0	1	0	0	1
F	5	12				0	0	0	1	0	0	1	1	0	1	1	1	1	0
G	6	20				1	0	1	1	1	1	0	0	1	1	1	1	1	1
H	7	21				1	0	1	1	1	1	0	0	0	0	1	0	0	1
I	8	22				1	0	1	1	1	1	0	1	0	1	1	1	1	0
J	9	100		1	1	0	1	1	1	1	1	1	0	1	1	1	1	1	1
K	10	101		1	1	0	1	1	1	1	1	1	0	0	0	1	0	0	1
L	11	102		1	1	0	1	1	1	1	1	1	1	0	1	1	1	1	0
M	12	110		1	1	0	0	0	1	0	0	1	0	1	1	1	1	1	1
N	13	111		1	1	0	0	0	1	0	0	1	0	0	0	1	0	0	1
O	14	112		1	1	0	0	0	1	0	0	1	1	0	1	1	1	1	0

P	15	120		1	1	1	0	1	1	1	1	0	0	1	1	1	1	1	1
---	----	-----	--	---	---	---	---	---	---	---	---	---	---	---	---	---	---	---	---

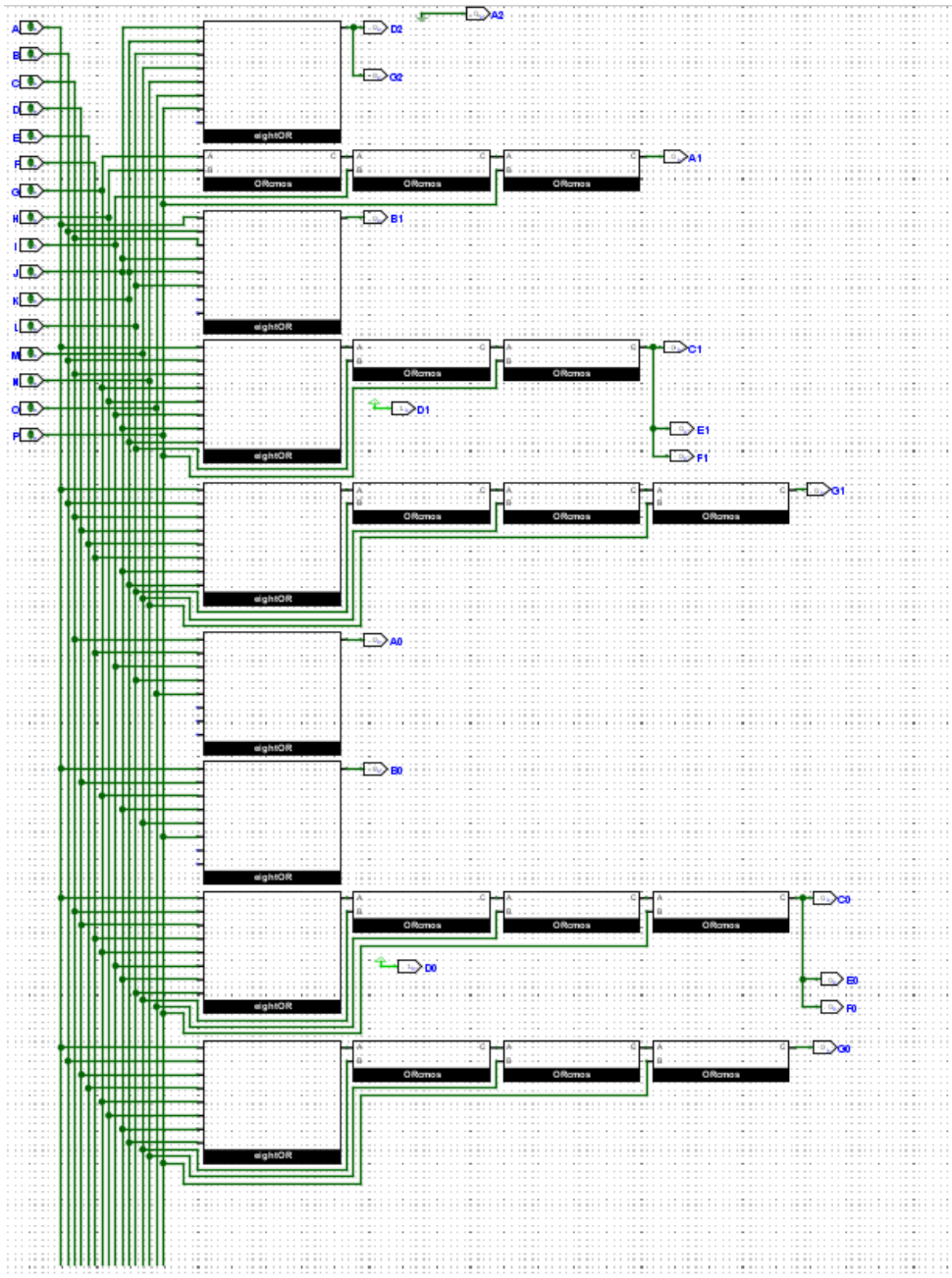


MUX: $\text{segOn} = (\text{signedMap()} * \text{sign}) + (\text{unsignedMap()} * (\text{not sign}))$

Suffix 0 = unsigned, suffix 1 = signed

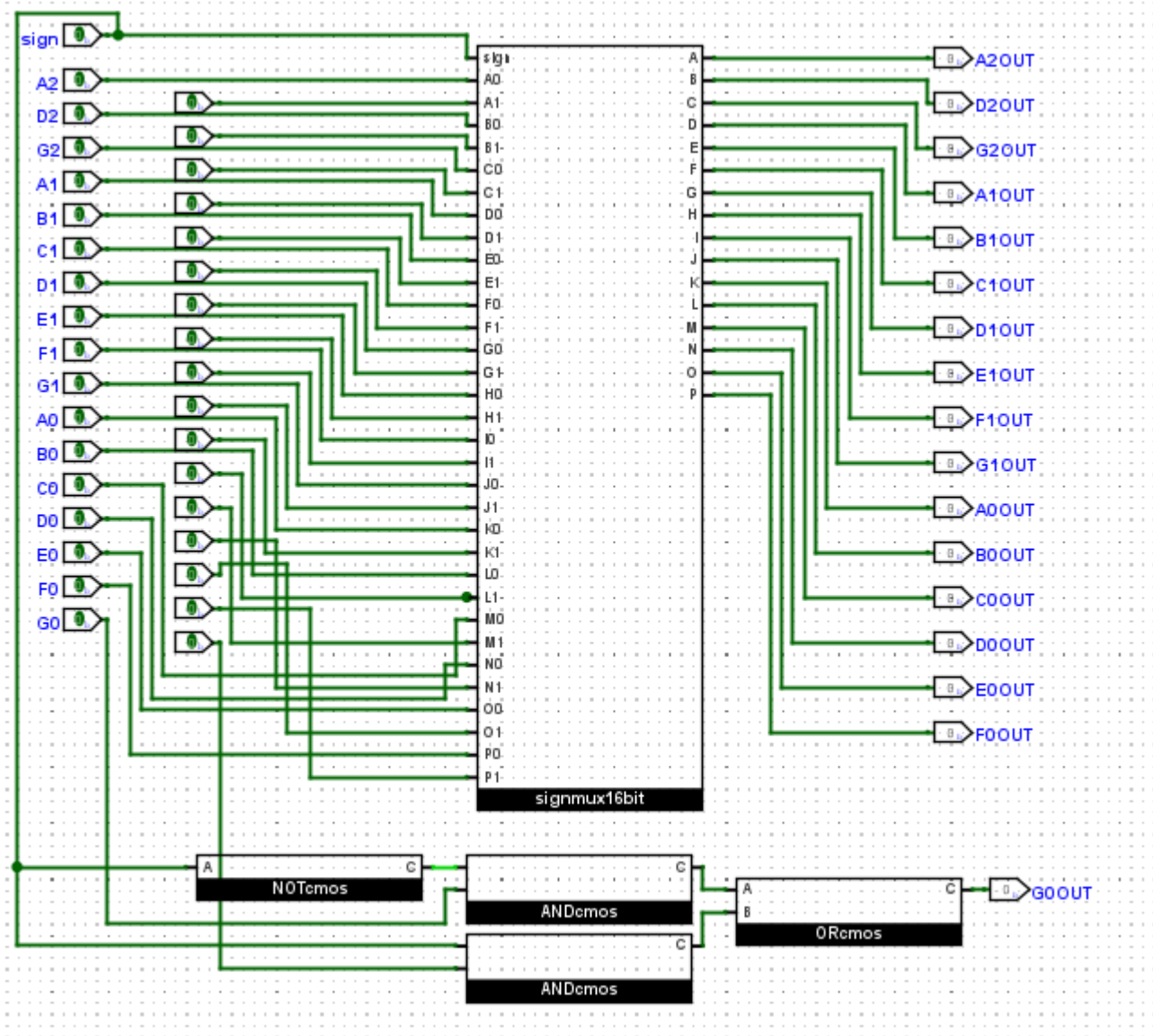

Put all 3 circuits above together:

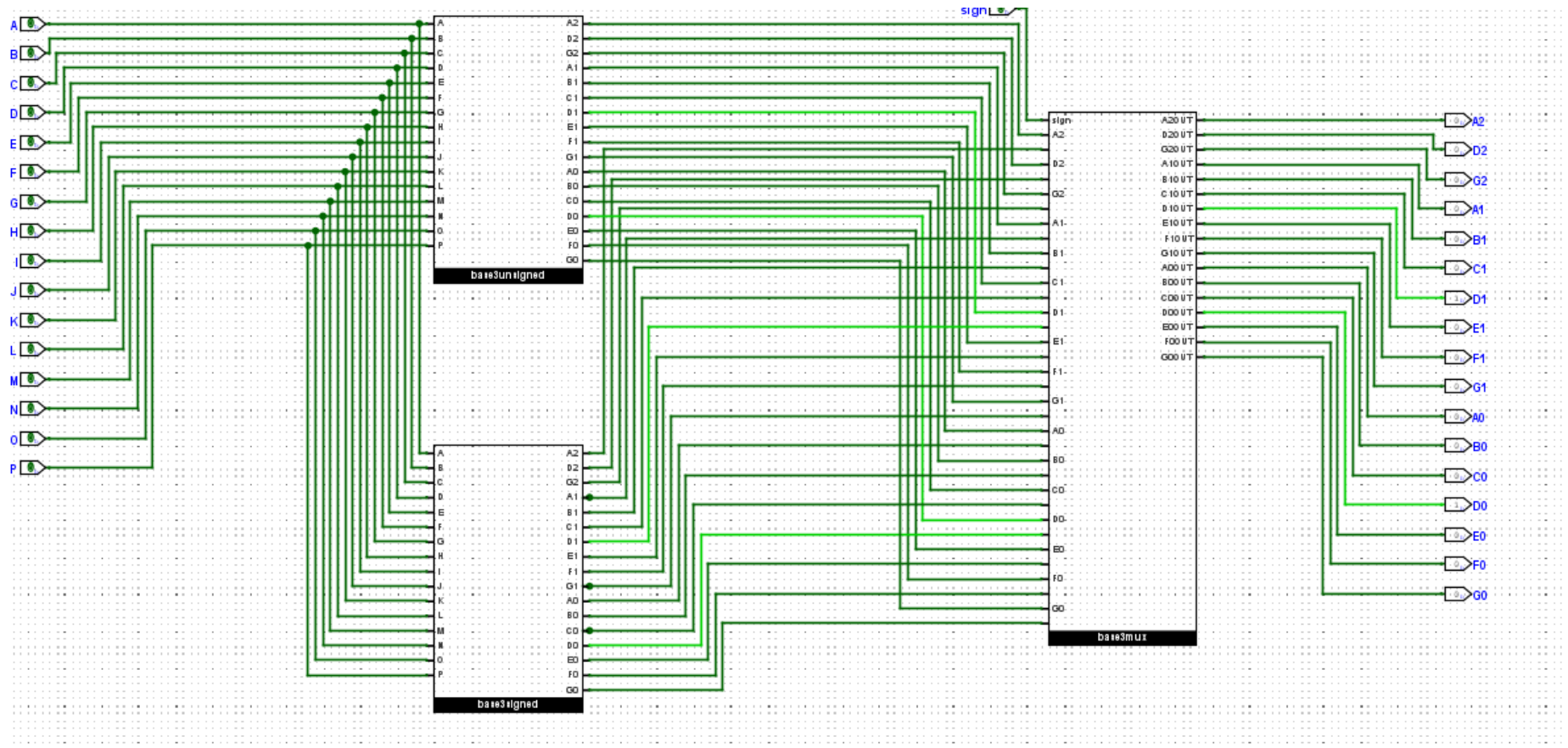

Output Overflow:


If overflow=1 then do not output anything

Boolean equation:

$\text{segOn} = \text{sevenssegmap()} * (\text{not overflow})$

For segments that are turned on to display Err:

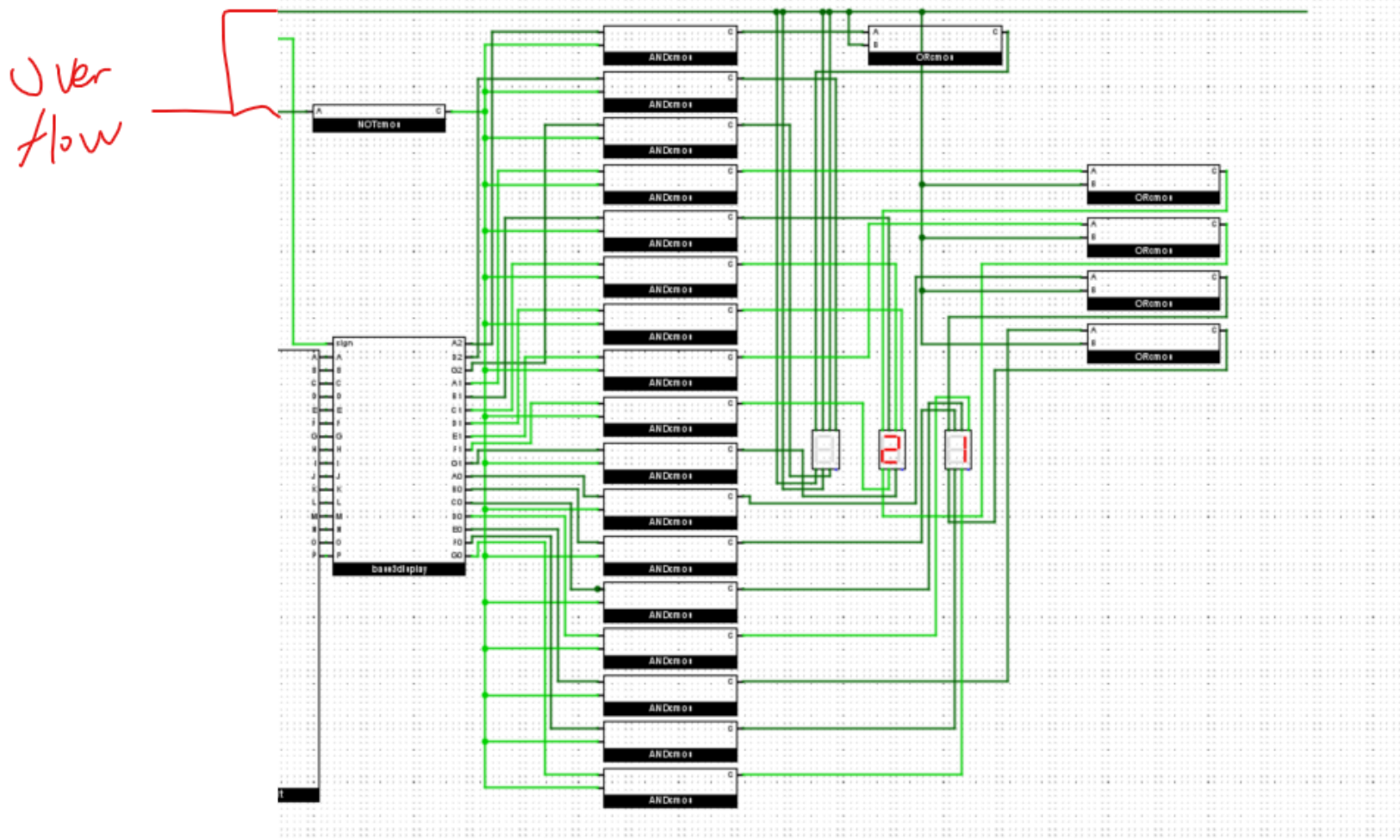$\text{segOn} = \text{sevenssegmap()} * (\text{not overflow}) + \text{overflow}$



Main Circuit:

